



- MCP23017's i2c bus allows up to 8 slaves by assigning different address via address pins
Will use shared bus and clock, SDA on PB3, SCL on PB2
- Tiva supplies 3.3V
MCP23017 will take 3.3V, but limited to 100kHz or 400kHz for i²c
Line driver will take logic from 3.3V i/o expander and supply 5V to 7seg displays
- 4.6kOhm (PCB v1) or 3.9k(PCB v2) resistors for SCL/SDA
- 330Ohm resistors for LEDs
- Potentiometers will use ADC on PB4&5
- ~~Purple/Green wires: GND, Yellow wires: VDD/Vcc or GPIO, Blue wires: +, Gray/White: SDA/SCL, Orange: GPIO (Cancelled breadboard, designed PCB)~~
- i2c scl/sda pullup resistors must be >=500 I think

$$R_p \geq \frac{V_{dd} - V_{OL}}{I_{OL}}$$

4.6k

SDA		V _{OL}	-	-	0.8	V	I _{OL} = 3.0 mA V _{DD} = 4.5V
-----	--	-----------------	---	---	-----	---	--

(3.3-1.8)/.003

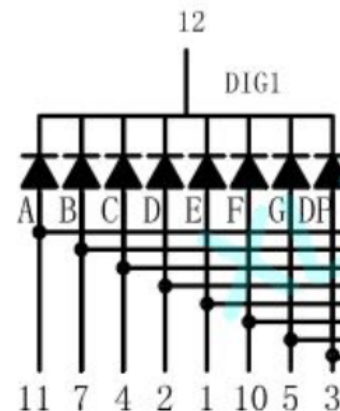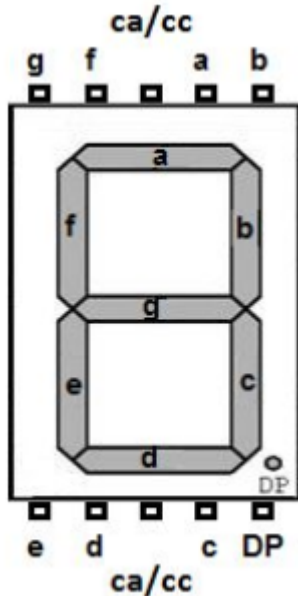

(Photos screenshotted from Google Images)

- 275 to 900Ohm resistors for LEDs
Top left: 220 (out of bounds)
Top right: 5x 330, 2x

Logs:

6/12/21 - sda/scl lines hooked up, 5v/3.3v/GND hooked up, i2c pullups, line driver power/enable/gnd hooked up, i/o expander connected to line buffer, i/o expander sda&scl&addresses wired, schematic finished
Still need to wire displays (w/ resistors), wire switches, connect all to microcontroller
(unknown date) - cancelled breadboard, doing PCB design

I2c addresses from I2CDetect on Beaglebone Black's linux

```
-- -- -- -- -- -- -- -- -- -- -- -- -- -- -- --
20 -- 22 -- 24 -- -- -- -- -- -- -- -- -- -- --
-- -- -- -- -- -- -- -- -- -- -- -- -- -- -- --
-- -- -- -- -- -- -- -- -- -- -- -- -- -- -- --
-- -- -- -- -- -- -- -- -- -- -- -- -- -- -- --
-- -- -- -- -- -- -- -- -- -- -- -- -- -- -- --
```